

# Chapter 4 Components and Circuits

[9 exam questions – 3 groups] G5, G6, G7

## Electrical Terms

**Impedance** is the **opposition** to the flow of current in an **AC** circuit

**Impedance** is measured in **Ohms**

**Reactance** is the **opposition** to AC caused by **capacitance or inductance**

**Reactance opposes** the flow of **AC** in an **inductor**

**Reactance opposes** the flow of **AC** in a **capacitor**

**Reactance** is measured in **Ohms**

## Electrical Properties

**Inductor reactance increases with frequency**

**Capacitor reactance decreases with frequency**

When the impedance of **load = source** the **maximum power** is delivered

To **maximize power transfer** use an **impedance matching transformer**

Insert an **LC network to match impedance** between circuits

A **transformer, Pi-network or transmission line** can be used for **impedance matching**

## Batteries, Resistors, Capacitors & Inductors

**Nickel-Cadmium batteries** provide **high discharge current** and low internal resistance

**10.5 volts** is the **minimum discharge voltage** of a standard **12 volt lead acid** battery

**Carbon-zinc** battery is not rechargeable **Never Charge**

**Resistor** resistance increases depending on **temperature coefficient**

A **wire-wound resistor's inductance** could make circuit performance unpredictable

A **thermistor** changes in **resistance** with **temperature** variations

**Electrolytic capacitors** are used in **power supply** circuits to filter the rectified AC

**Ceramic capacitors** are **low cost** compared to other types

**High capacitance for given volume** is an advantage of an electrolytic capacitor

**Low equivalent series resistance for capacitors** used to filter the DC

**Lead inductance** in a capacitor **reduces** effectiveness at **VHF** and above

**Filter choke smoothes DC output** from the rectifier in a power supply

**Inter-turn capacitance** in an inductor may cause **self resonant** at some frequencies

**Mutual inductance** between inductors causes **unwanted coupling** between circuits

A ferrite core toroidal has; **large inductance, freq optimized properties, magnetic field stay in core**

Place windings solenoid inductors at **right angles** to **minimize mutual inductance**

## Diodes & Light Emitting Diode

**0.3 volts** junction threshold voltage of a **germanium diode**

**0.7 volts** junction threshold voltage of a **conventional silicon diode**

**Diodes in parallel** to increase current capacity need **current limiting resistors**

The **peak-inverse-voltage** is max voltage the in the **non-conducting direction**

**Peak inverse voltage & average forward current** must not be exceeded for **silicon diode** rectifiers

**Schottky diodes** (RF switching circuit) have **lower capacitance** compared to a silicon diode

An LED is **Forward Biased** when emitting light (conducts)

An **incandescent** indicator has **high power consumption** compared to an LED

A **liquid crystal display** requires ambient or back **lighting**

## Transistor & Vacuum Tubes

**Saturation and cut-off regions** are **stable operating** points for a bipolar transistor used in a logic circuit

**Cases of power transistors** are **insulated** to avoid shorting the collector or drain to ground

A **MOSFET gate** is **separated from the channel** with a thin insulating layer

A **Field Effect Transistor** is like a vacuum tube in its general operating characteristics

**Control grid of a triode tube** **regulates the flow of electrons** between cathode and plate

A **screen grid** in a vacuum tube **reduces grid-to-plate capacitance**

# Chapter 4 Components and Circuits

[9 exam questions – 3 groups] G5, G6, G7

## Transformers

**Mutual inductance** causes a voltage to appear across the **secondary winding** of a transformer

The **primary** of a transformer is normally connected to the **incoming source**

The transformer output = **Input x (Np/Ns)**

The transformer output = **Input x Square Root of (Pimp/Simp)**

## Digital Circuits

**Binary** "ones" and "zeros" are easy to represent with an "on" or "off" state

**AND gate** output is high only when **both** inputs are high

**NOR gate** output is low when **either or both** inputs are high

**Eight** states in a **3-bit binary** counter

A **shift register** is a clocked array that **passes data in steps** along the array

**Complex digital circuitry** can often be replaced by a **Microcontroller**

## Integrated Circuits

**Linear voltage regulator** is an analog integrated circuit

Integrated circuit **operational amplifier** is an **analog** device

MMIC >> **Monolithic Microwave Integrated Circuit**

ROM >> **Read Only Memory**

**"NON-VOLATILE"** memory information is maintained even if power is removed

A microprocessor is a **computer on a single integrated circuit**

**CMOS** integrated circuits have **lower power consumption** compared to TTL

## Resistors, Inductors & Capacitors

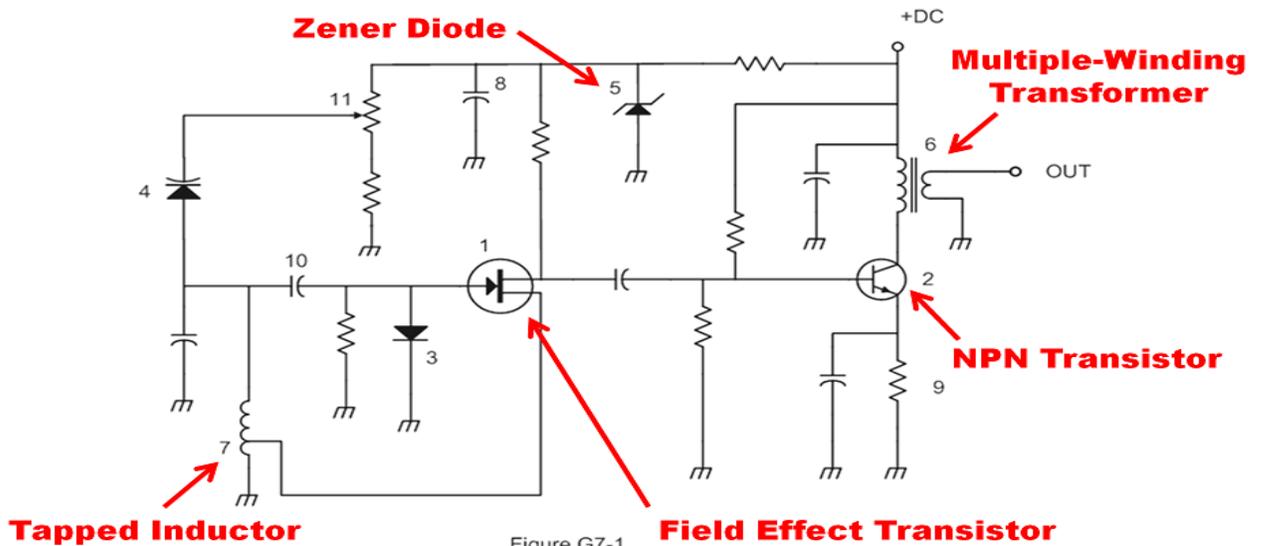


Figure G7-1

# Chapter 4 Components and Circuits

[9 exam questions – 3 groups] G5, G6, G7

## Resistors, Inductors & Capacitors (Con't)

**Resistors in series** = resistor values added

**Equal Resistors in parallel** = resistor value / number of resistors

**Resistors in parallel** = the reciprocal of (the sum of all the reciprocal resistor values)

**Equal Inductors in parallel** = inductor value / number of inductors

**Inductors in parallel** = the reciprocal of (the sum of all the reciprocal inductor values)

**Inductors in series** = inductors values added

**Capacitors in parallel** = capacitor values added

**Equal Capacitors in series** = capacitor value / number of capacitors

**Capacitors in series** = the reciprocal of (the sum of all the reciprocal capacitor values)

Inductors or Resistors in Parallel

Inductors or Resistors in Series

Capacitors in Series

Capacitors in Parallel

$$L = \frac{1}{\frac{1}{L} + \frac{1}{L} + \dots + \frac{1}{L}}$$

$$L = L + L + \dots + L$$

$$C = \frac{1}{\frac{1}{C} + \frac{1}{C} + \dots + \frac{1}{C}}$$

$$C = C + C + \dots + C$$

## Ohm's Law, Power, Vpp, RMS, PEP

$$E = I \times R$$

$$I = E / R$$

$$R = E / I$$

$$P = E \times I$$


$$P = I^2 \times R$$

$$PEP = [(V_{pp}/2) \times 0.707]^2 / R$$

$$V_{pp} = \text{Voltage Peak to Peak} = 2 (1.41 \times \text{RMS})$$

$$\text{RMS} = \text{Peak} \times 0.707$$

$$I = P / E$$

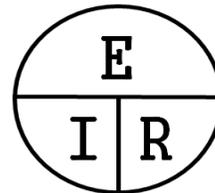

**Total current** in each branch of a **parallel** circuit equals **sum of the branches**

The **RMS value** of an AC signal is the **power dissipation** as a DC voltage of the **same value**

The ratio of **peak** envelope power to **average** power for an **unmodulated carrier** is **1.00**

## Decibel (dB)

$$+1 \text{ dB} = 20.5\% \text{ of } X \quad +3 \text{ dB} = 2X \quad +6 \text{ dB} = 4X \quad +10 \text{ dB} = 10X$$

## Test and Measurement Equipment

An **oscilloscope** contains **horizontal and vertical channel** amplifiers

An oscilloscope can **measure complex waveforms**

An oscilloscope can **check the keying waveform of a CW transmitter**

The attenuated TX RF is connected to **the vertical of an oscilloscope to check RF envelope**

A **high input impedance voltmeter** decreases the **loading on circuits** being measured

A **digital voltmeter** has **better precision** than an analog meter

A **field strength meter** can be used for **close-in radio direction-finding**

A **field strength meter** can be used for **relative RF output** on antennas and transmitters

A **field strength meter** can be used to **radiation pattern** of an antenna

An **antenna analyzer** is used for **antenna and feed line SWR measurements**

An **antenna analyzer** is used to **determine the impedance of a coaxial cable**

**Strong signals** can affect the **accuracy of antenna analyzer** measurements

An **analog** readout may be **preferred** when **adjusting tuned circuits**

**Standing wave ratio (SWR)** can be determined with a **directional wattmeter**

**Transmitter Linearity** performance is determined by a **two-tone test**

Two **non-harmonically related audio signals** are used to conduct a **two-tone test**

# Chapter 4 Components and Circuits

[9 exam questions – 3 groups] G5, G6, G7

## Connectors

**Computer and transceiver** might be connected using a **USB interface**

**DE-9 connectors** would be a good choice for a **serial data port**

**Keyed connectors** reduce chance of **incorrect mating**

**DIN connector** is a multiple circuit connector suitable for audio and control signals

**RCA Phono** connectors are commonly used for **audio signals**

**PL-259** connectors are commonly used for RF service at **frequencies up to 150 MHz**

**SMA connector** is a small threaded connector suitable for signals up to several GHz

**N connector** is a moisture-resistant RF connector useful to 10 GHz

## Power Supplies

The **peak-inverse-voltage** across the rectifiers in a **full-wave PS = PS output voltage**

The **peak-inverse-voltage** across the rectifiers in a **half-wave PS = 2 X PS output voltage**

**360 degrees** of the AC cycle is converted to DC by a **full-wave rectifier**

**180 degrees** of the AC cycle is converted to DC by a **half-wave rectifier**

The OP waveform of a **full-wave rectifier** = DC **pulses 2X freq** of the AC input

Capacitors and inductors are used in a **power-supply filter network**

A power-supply **bleeder resistor** discharges the filter capacitors

A **switch-mode PS high freq operation** allows the use of smaller components